 


## Chapter 4 The processor: Datapath & Control




- Two implementations of MIPS instruction architecture
  - Single cycle implementation
    - Datapath & Control
  - Pipeline implementation
    - Datapath & Control
    - Data dependence/Hazard
- Consider only the core of MIPS inst. Set
  - memory-reference inst. lw, sw
  - ALU inst. add, sub, and or, slt -- R-type
  - branch inst. beq, j

# The Performance Perspective

- Performance of a machine is determined by:
  - Instruction count
  - Clock cycle time
  - Clock cycles per instruction
- **Processor design (datapath and control) will affect:**
  - **Clock cycle time**
  - **Clock cycles per instruction**
- Single cycle processor:
  - A simple start to understand more complicated pipeline implementation



 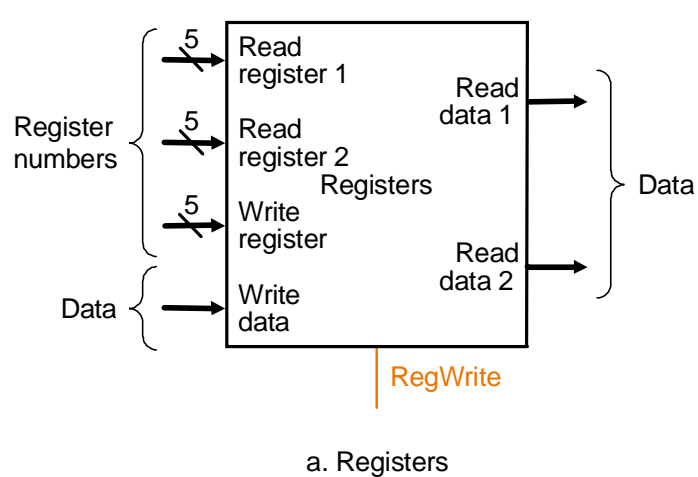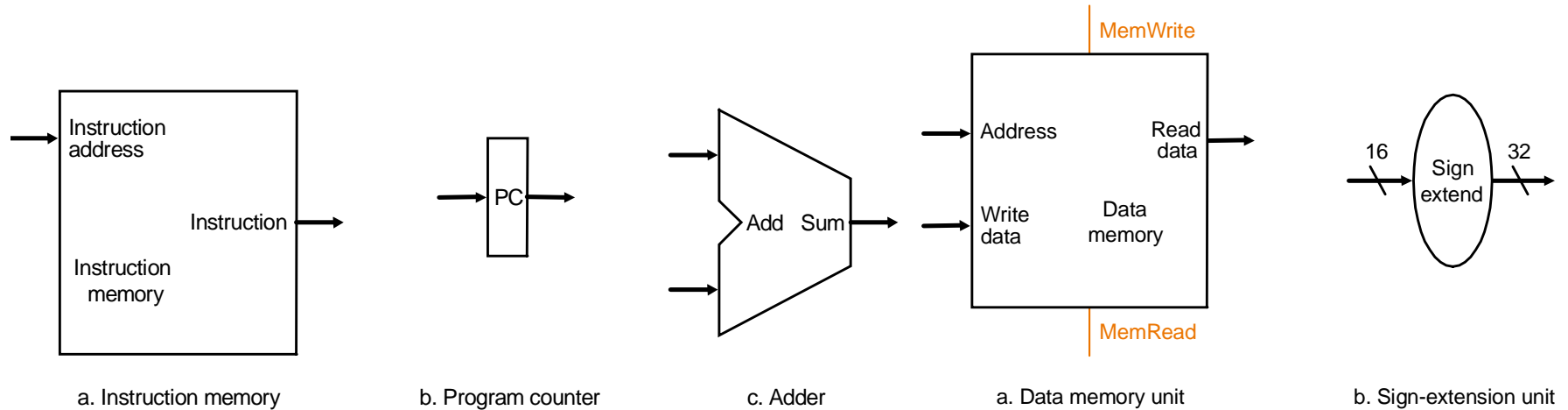
# Functional Units for Implementing instructions



## MIPS ALU Functions

Control	Funct	Result
0000	AND	aANDb
0001	OR	aORb
0010	add	a+b
0110	sub	a-b
0111	slt	1 if a<b

Zero flag:

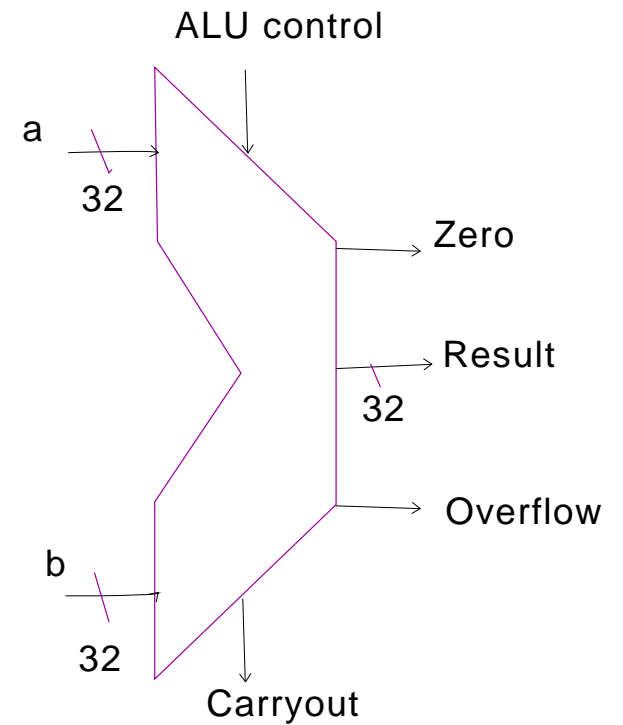


## Basic Idea of Datapath Design

- Design a datapath for each type of instruction
  - R
  - lw
  - sw
    - Combine lw and sw
  - beq
- Combine all

## Datapath for R-type

- Example: add \$3, \$4, \$5
- Basic steps
  - fetch instruction
  - select registers (rs, rt),
  - ALU operation on two data, need ALU
  - write back registers

## Single-Cycle: Datapath for R-type

 

## Datapath for Load Word

- Basic steps: example: `lw $3, 300($4)`
  - fetch instruction
  - select a register (rs)
  - calculate address, need ALU
  - access memory (read memory)
  - write register file



## Datapath for Store Word

- Basic steps: example: `sw $3, 300($4)`
  - fetch instruction
  - select a register (rs)
  - calculate address, need ALU
  - access memory (write memory)

## Combining datapaths of lw & sw


- `rt`: write address for lw, read address for sw.
- Register write control signal.

## Datapath for beq

- Basic steps
  - fetch the instruction
  - select registers
  - test condition, calculate branch address (need additional ALU)

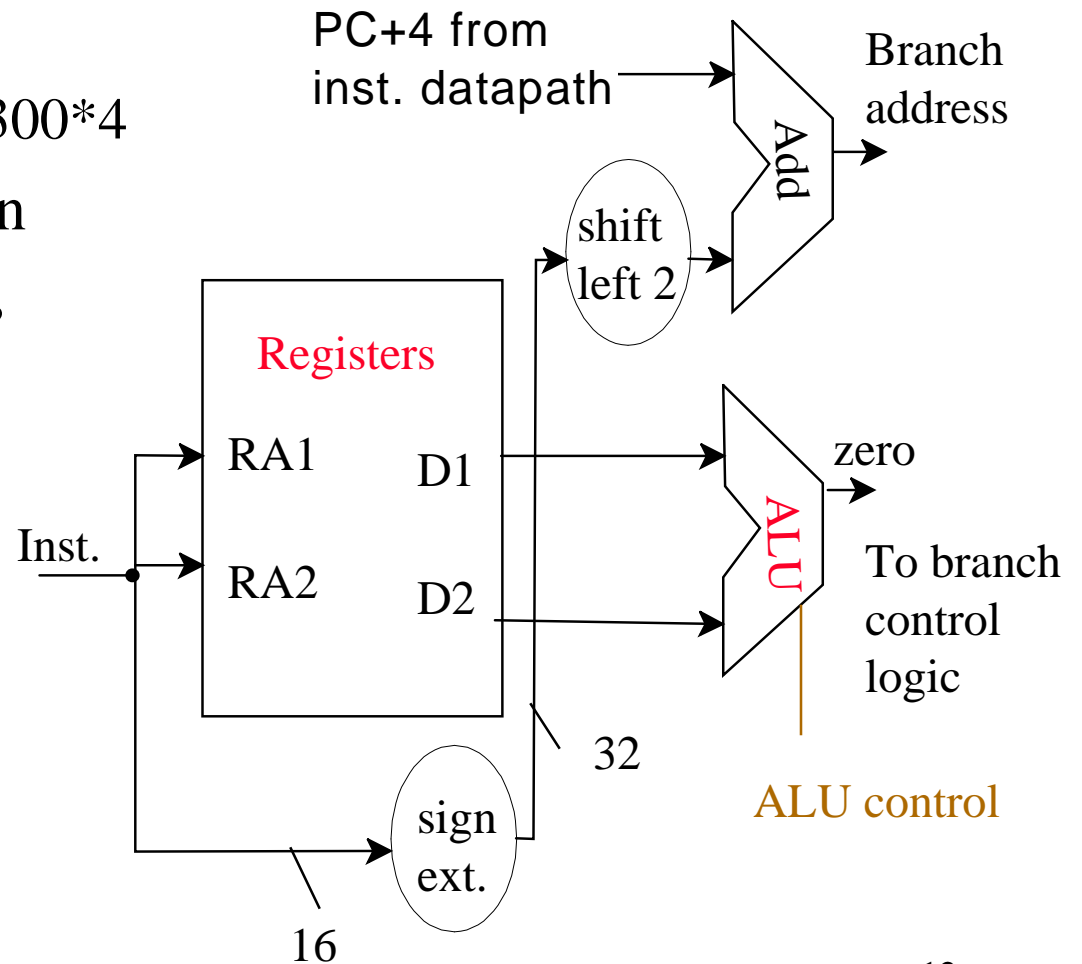
## Datapath for Branch Inst.

- beq \$1, \$2, 300
  - if (\$1=\$2) goto PC+4+300\*4
- ALU for branch condition
- Adder for branch address
- Shift left 2: X by 4
- Zero: control logic to decide if branch.



 
## Creating a Single Datapath for All Inst.

- Combine datapaths for R-type, memory inst. and branch inst.
  - using multiplexers
  - without duplicating common functional units.
- As an example, combine R-type and memory type datapaths
- Final goal: combine all types of datapaths



R-type data path

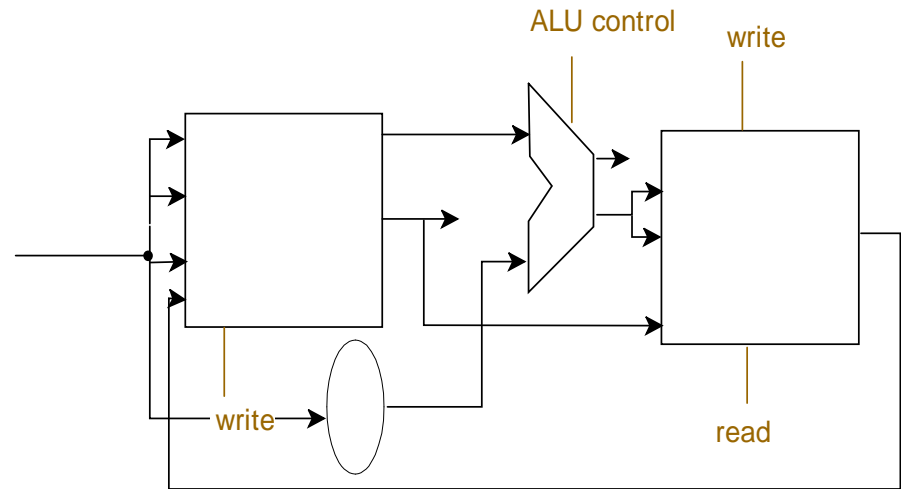

Memory type datapath


### Key Differences:

2nd input to ALU

Value written into register file

Register write address


# Simple Datapath for Single Cycle

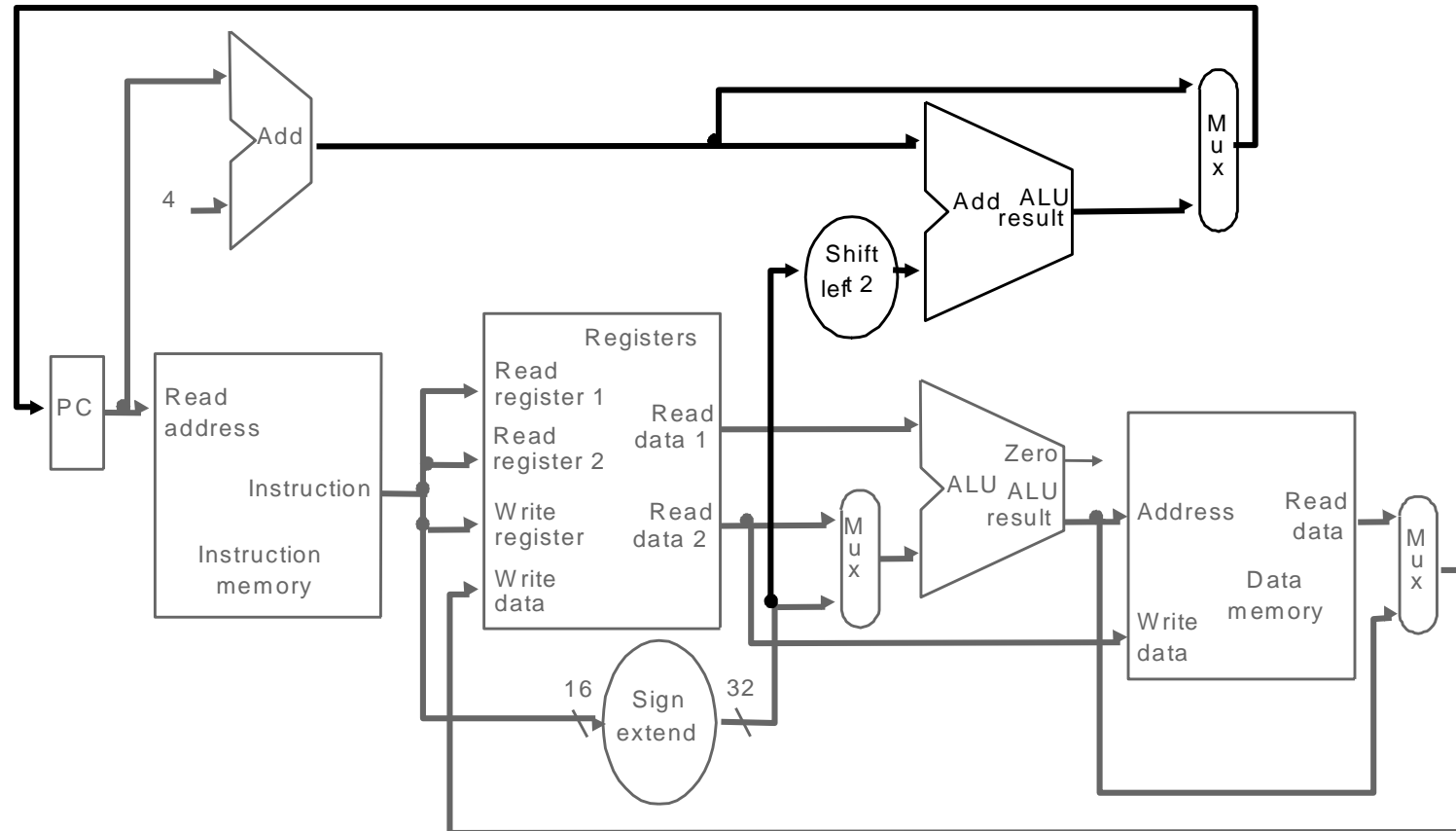

Can execute basic instructions in a single clock cycle

No resource can be used more than once during a single cycle


# Control?

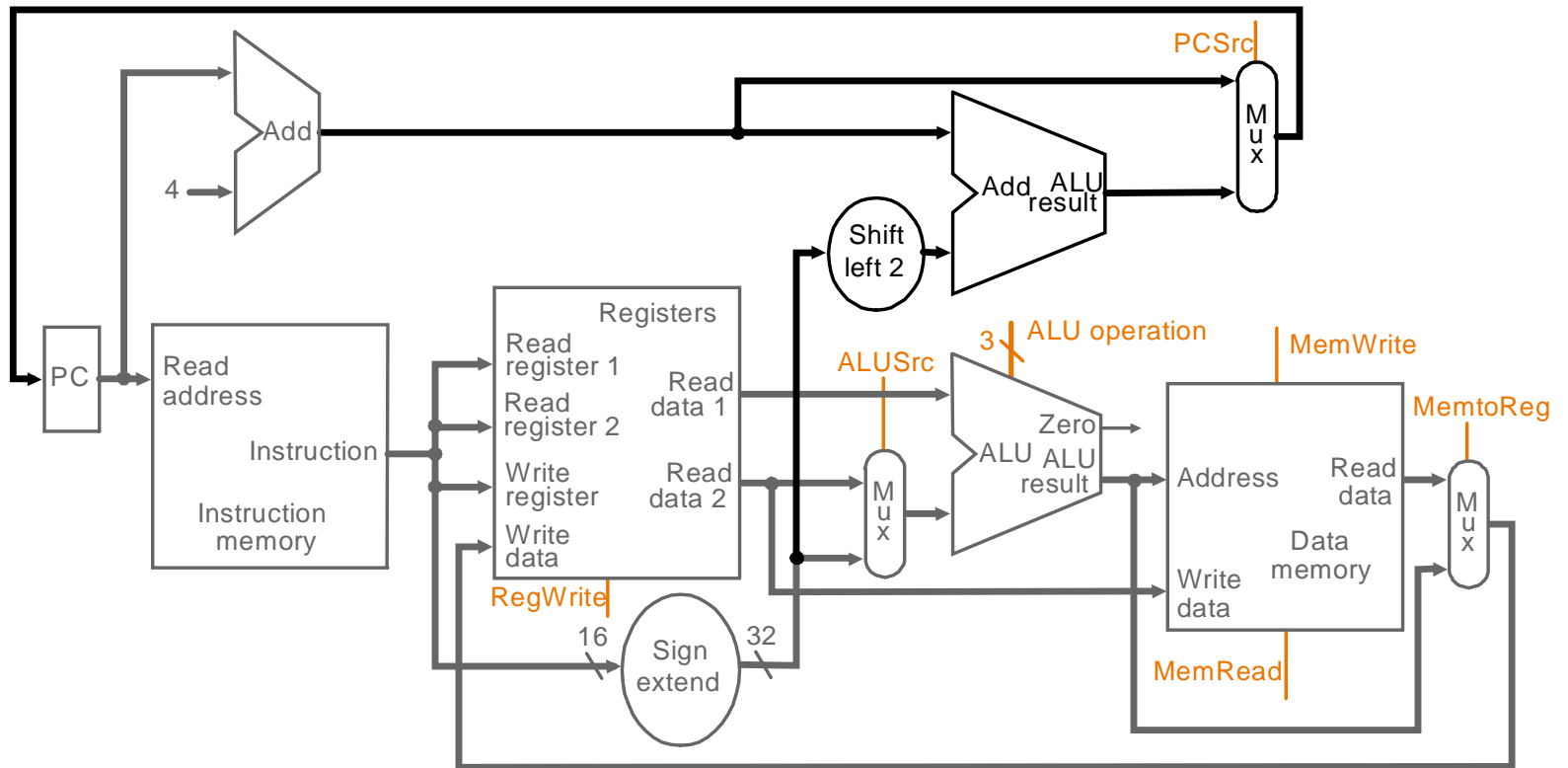



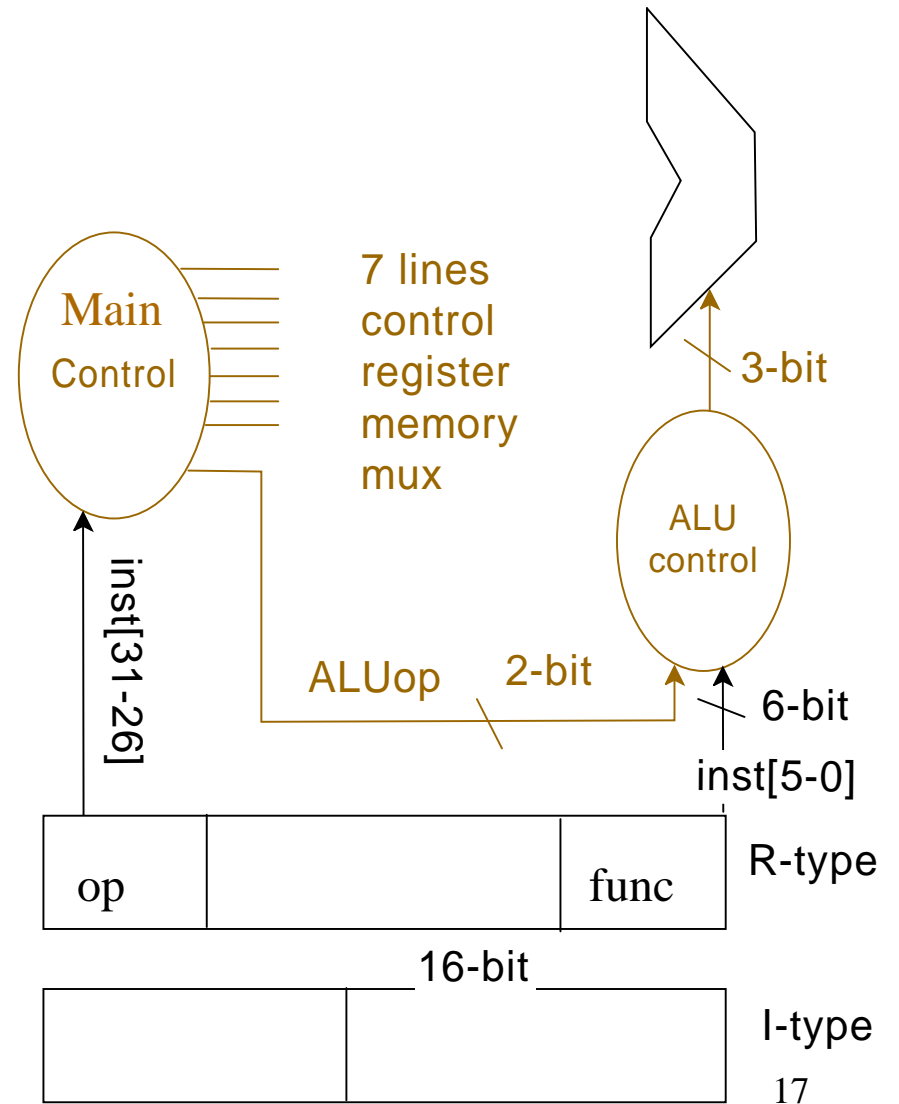
# Single-Cycle: Control

- Main control:
  - input: 6-bit from op field
  - output: 9 control lines
- ALU control:
  - input: ALUop + 6-bit (function field)
  - output: 3 lines
  - for I, J type, ALU control depends on only ALUop



# Control

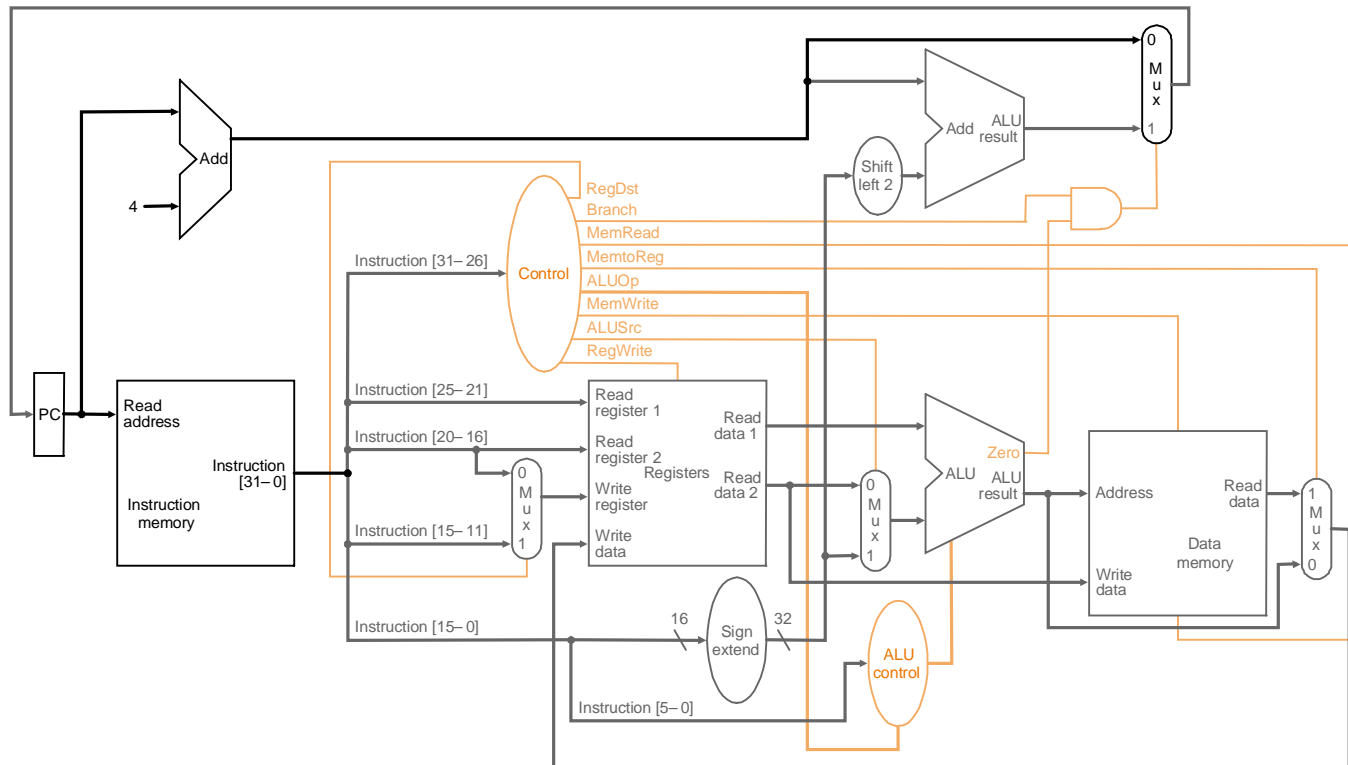


Instruction	RegDst	RegWrt	Memto-Reg	Brch	Mem Read	Mem Write	ALUSrc	ALUOp1	ALUp0
R-format									
lw									
sw									
beq									

## Main Control Unit -- Definitions of Control Signals


Signal Name	Effect when deasserted	Effect when asserted
MemRead	None	Data put on read dataoutput
MemWrite	None	Write data into memory
RegWrite	None	Write register
ALUSrc	2nd ALUinput from register file	2nd ALUinput from inst[15-0]
PCSrc	PC = PC+4	PC = branch address
MemtoReg	result of ALU is sent	data in memory is sent
RegDst	inst[20-16] (rt) provides register write address	inst[15-11] (rd) provides register write address

PCsrc = branch AND zero

# Single cycle control

 

# ALU Control

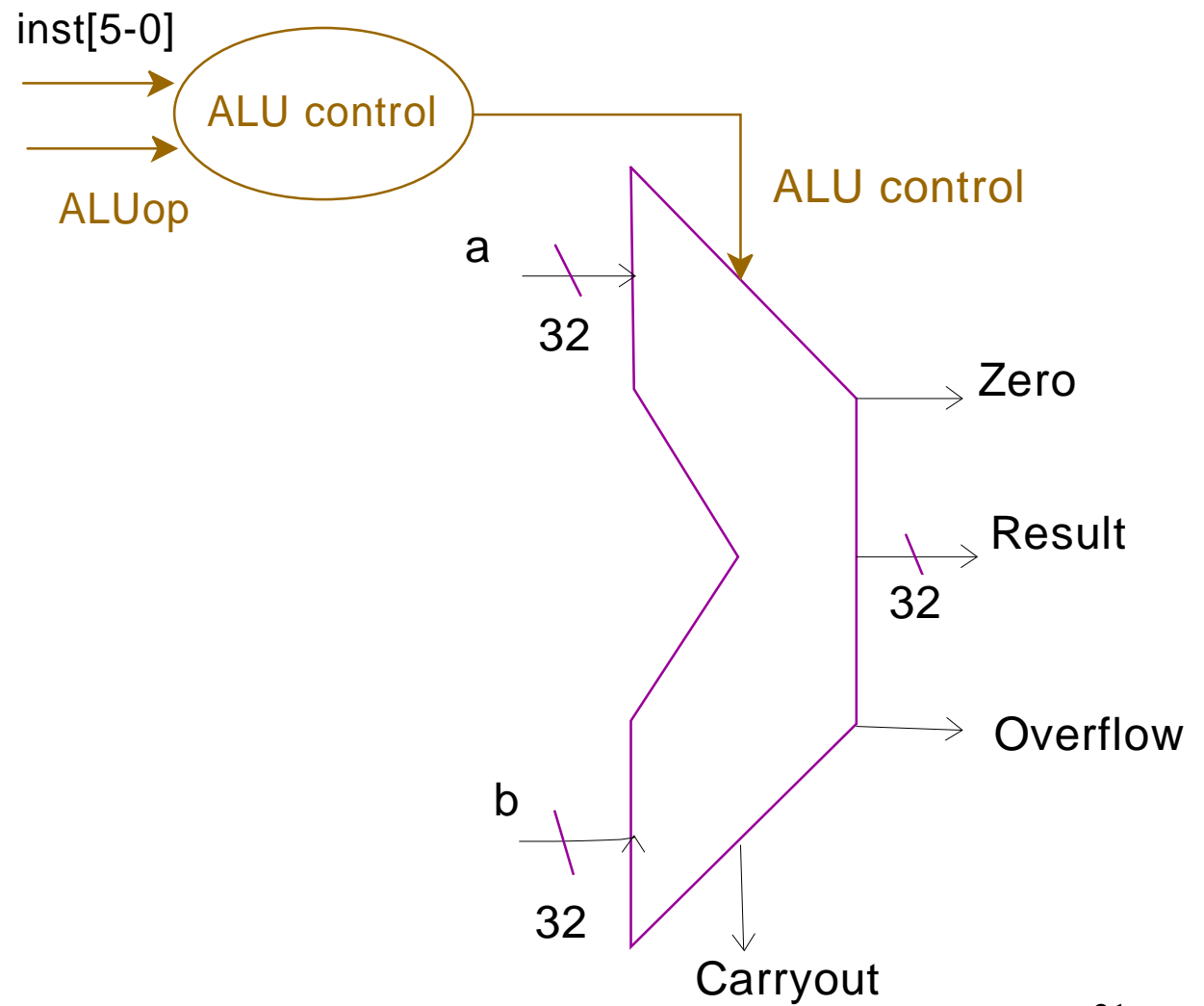

ALU Control	Funct
000	AND
001	OR
010	add
110	sub
111	slt

## ALU Control, Truth Table

Inst opcode	Inst. operation	Desired ALU act.	ALUop	Function code	ALU control
lw	load word		00	xxxxxx	
sw	store word		00	xxxxxx	
beq	branch equal		01	xxxxxx	
R-type	add		10	10 0000	
R-type	sub		10	10 0010	
R-type	AND		10	10 0100	
R-type	OR		10	10 0101	
R-type	slt		10	10 1010	


\*ALUop: output of main control

R-: ALUop=10,

lw/sw: ALUop=00

\*ALU Control: combinational logic  
8 inputs, 3 output.
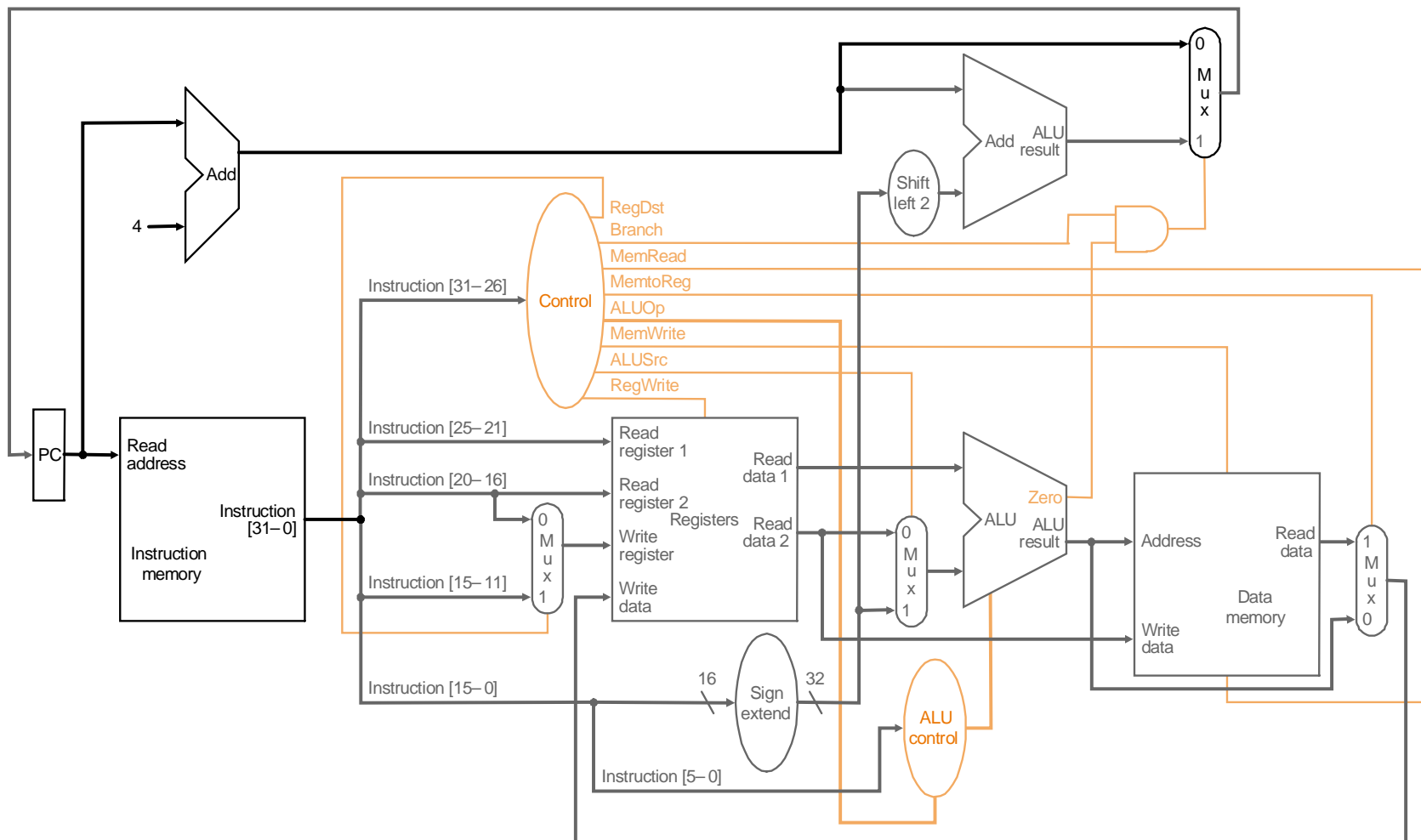
# Execution of *add \$1, \$1, \$3* in roughly 4 steps



## Single-Cycle: J-type

- So far, our datapath can handle R-type, lw/sw, beq

- How about J-type?

- J-type      j   L1  
                  jal L1

31-26

25-0


–




address =  $a_{25} \dots a_0$       current PC + 4 =  $PC_{31}PC_{30} \dots PC_0$

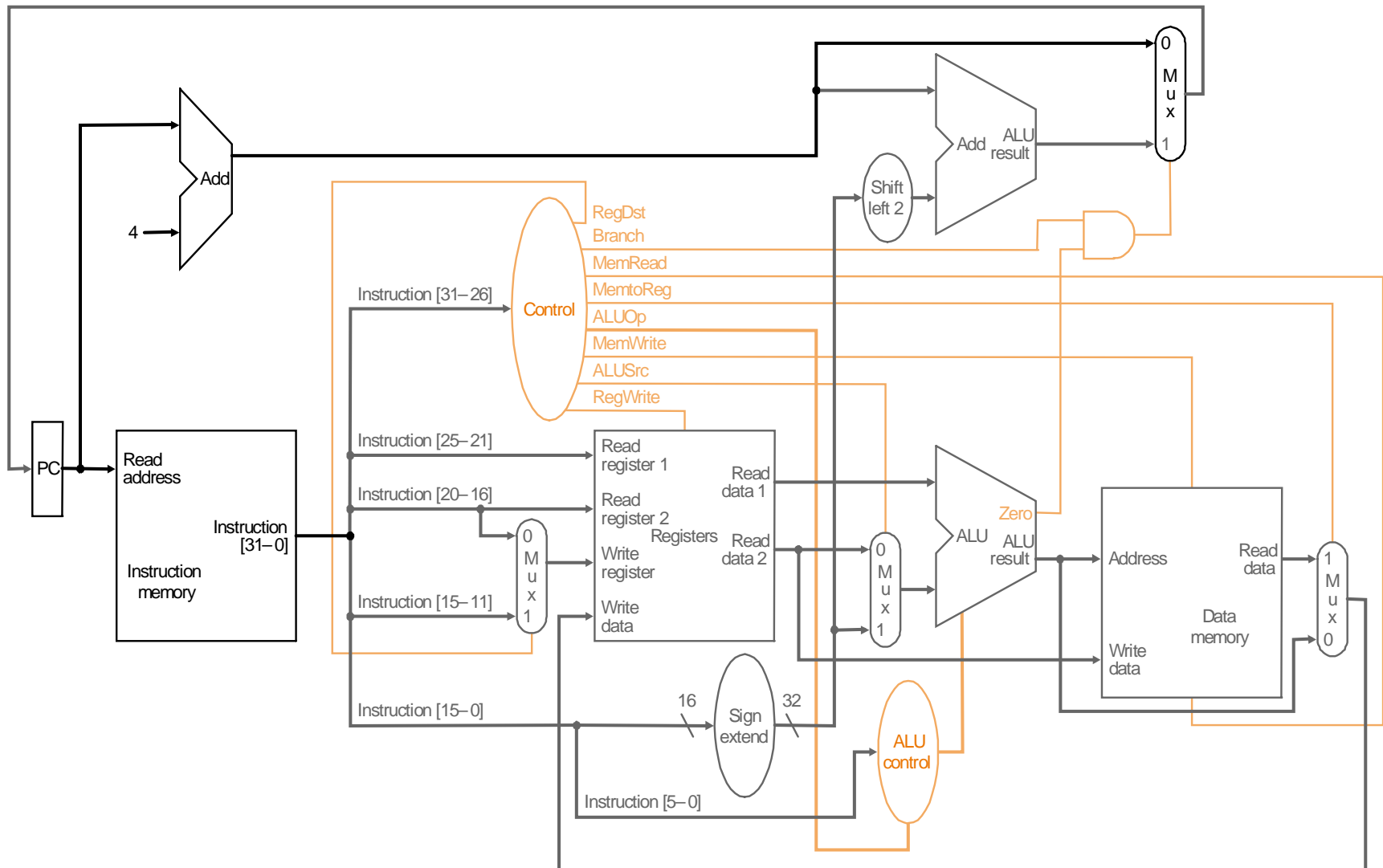Actual address L1 =  $pc_{31} pc_{30} pc_{29} pc_{28} a_{25} \dots a_0 00$




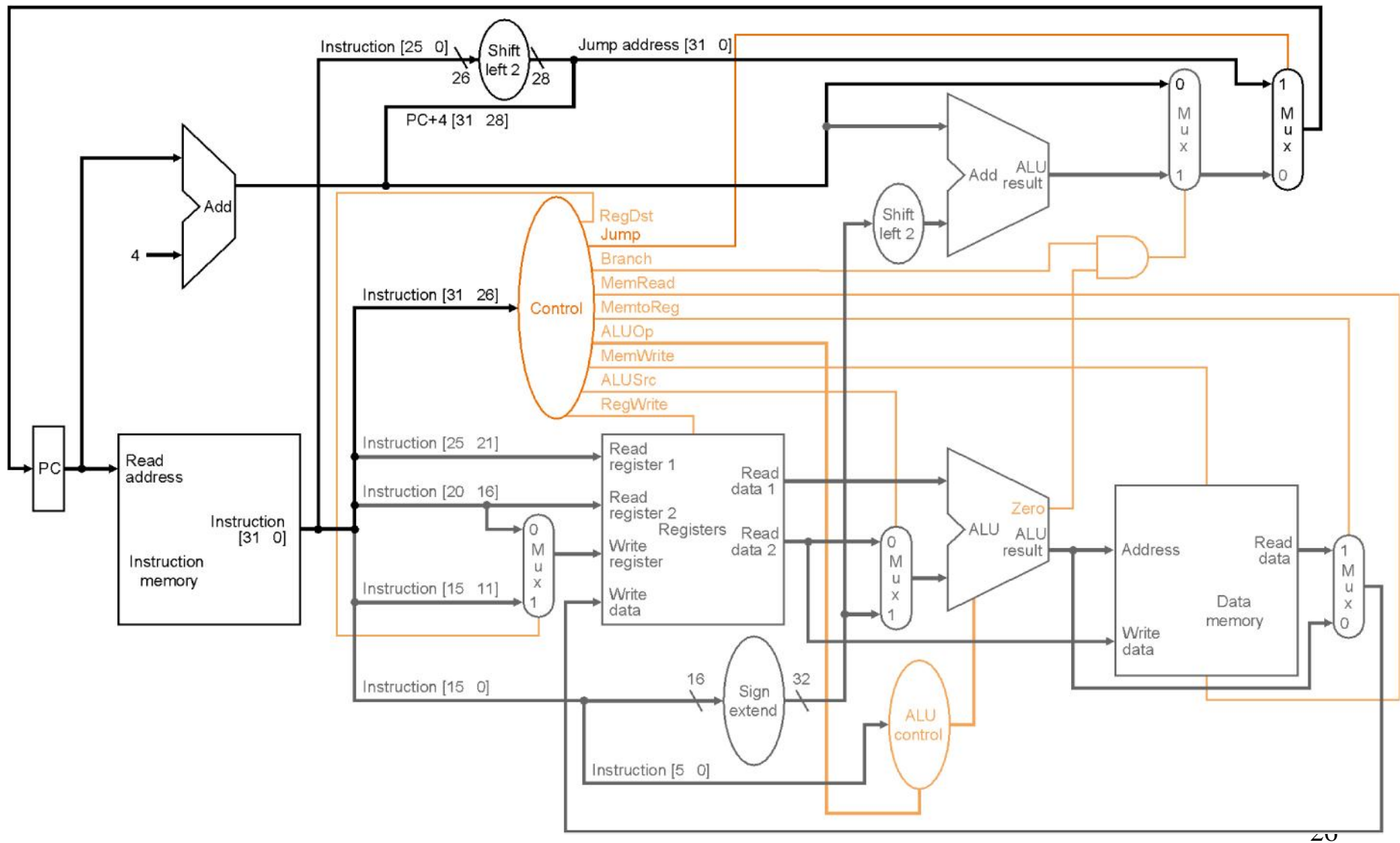
## Single-Cycle: Datapath + Control including jump inst



## Single-Cycle: Summary

- How to construct datapath for R-type, lw/sw, beq, j
- How to construct the control
  - ALU control
  - main control
- How the datapath + control to execute instruction

# Execution (cycle) Time Analysis

Arithmetic & Logical




Load



← Critical Path →

Store

 

Branch



- Cycle time  $\geq$  the critical path length
- Long Cycle Time
  - All instructions take as much time as the slowest

Exercise: Can MemtoReg be eliminated and replaced by MemRead?

	RgDst	Jp	Brnch	MemRd	MemtoRg	ALUop	MemWrt	ALUSrc	RegWrt
<i>lw</i>	0	0	0	1	1	00	0	1	1
<i>sw</i>	x	0	0	0	x	00	1	1	0
<i>R</i>	1	0	0	0	0	10	0	0	1
<i>beg</i>	x	0	1	0	x	01	0	0	0
<i>Jp</i>	x	1	0	0	x	xx	0	x	0
			B						

Exercise: What would be the cycle time for the following cases?

- Assume
  - ALU delay=2ns,
  - Adder (PC+4) delay=x ns,
  - Adder (branch address) delay = y ns
- $X=3, y=3$
- $x=5, y=5$
- $x=1, y=8$